

Name(in Arabic)

Student No.

Section

1. A 4-pole, dc generator having a total number of conductors of 600 and a flux per pole of 0.01 Wb. Total number of slots = 20 and a speed of 1000 rpm. Neglect the winding resistance. Find the induced emf and the torque in case a load of 10Ω is connected across the terminals for the following cases:

8 marks

- (i) Lap, retrogressive, duplex, double layer winding

$$a = 4 \times 2 = 8 \quad k = \frac{600 \times 4}{2\pi \times 8} = \frac{150}{\pi}$$

$$E_a = \frac{150}{\pi} \times 0.01 \times 1000 \times \frac{2\pi}{60} = 50 \text{ V}$$

$$T = \frac{50 \times 50}{\frac{10}{\frac{2\pi}{60} \times 1000}} = 2.387$$

EMF = 50

Torque = 2.387 Nm

- (ii) Lap, progressive, simplex, double layer winding

$$a = 4 \quad k = \frac{600 \times 4}{2\pi \times 4} = \frac{300}{\pi}$$

$$E_a = \frac{300}{\pi} \times 0.01 \times 1000 \times \frac{2\pi}{60} = 100 \text{ V}$$

$$T = \frac{100 \times 100}{\frac{10}{\frac{2\pi}{60} \times 1000}} = 9.55 \text{ Nm}$$

EMF = 100

Torque = 9.55 Nm

- (iii) Wave, progressive, simplex, single layer

$$a = 2 \quad k = \frac{600}{\pi}$$

$$E_a = \frac{600}{\pi} \times 0.01 \times 1000 \times \frac{2\pi}{60} = 200 \text{ V}$$

$$T = \frac{200 \times 200}{\frac{10}{\frac{2\pi}{60} \times 1000}} = 38.197$$

EMF = 200 V

Torque = 38.197 Nm



- (iv) Wave, retrogressive, simplex, double layer winding

$$a = 2 \quad \text{Same as (iii)}$$

EMF = 200 V

Torque = 38.197 Nm

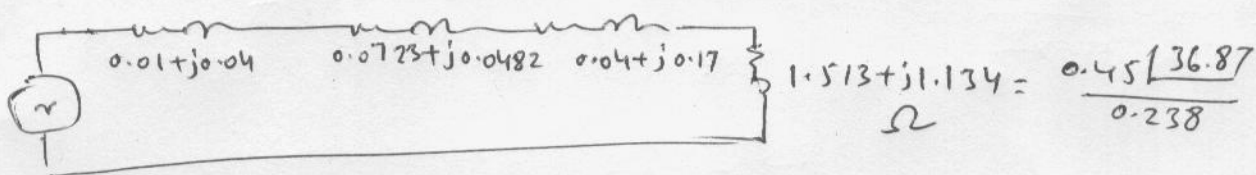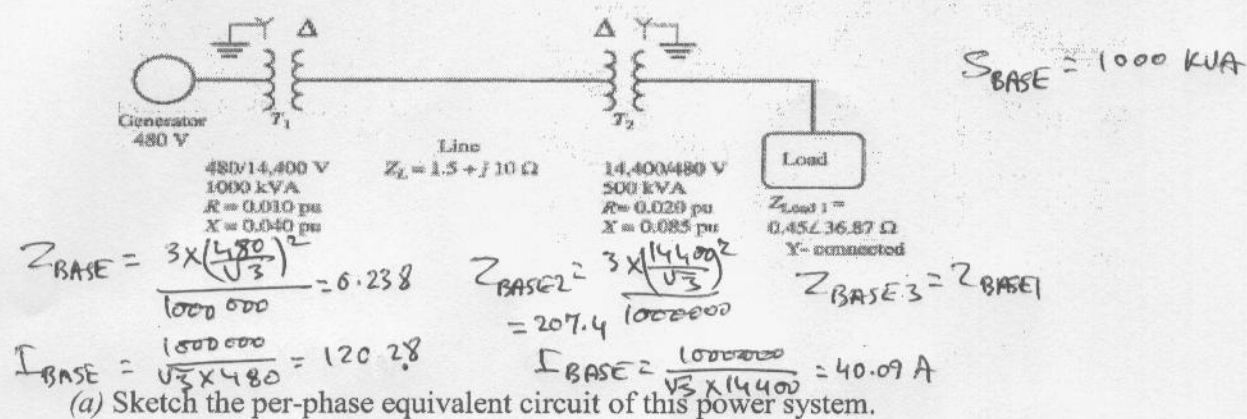2. The figure below shows a power system consisting of a three-phase 480-V 60-Hz generator supplying a load through a transmission line with a pair of transformers at either end. 8 marks



(b) Find the real power P , reactive power Q , and apparent power S supplied by the generator. What is the power factor of the generator?

0.5
0.5
0.5
0.5

$$Z_{eq} = (0.01 + 0.04 + 0.0723 + 1.513) + j(0.04 + 0.17 + 0.0482 + 1.134)$$

$$= 1.5702 + j1.3922 = 2.099 \angle 41.6^\circ$$

1

$$I = \frac{1}{2.099 \angle 41.6} = 0.4765 \angle -41.6 \text{ A}$$

0.5
0.5
0.5
0.5

$$P = 1 \times 0.4765 \cos 41.6 = 0.356 \text{ pu} \rightarrow 356 \text{ kW}$$

$$Q = 1 \times 0.4765 \sin 41.6 = 0.316 \text{ pu} \rightarrow 316 \text{ kVAR}$$

$$S = 1 \times 0.4765 = 0.4765 \text{ pu} \rightarrow 476.5 \text{ kVA}$$

(c) What are the transmission losses (transformer plus transmission line losses) in this system

1

$$P_{loss} = 0.4765^2 [0.01 + 0.04 + 0.0723] = 0.0577 = 0.0131 \text{ p.u.}$$

$$= 0.0131 \times 1000000 = 13.1 \text{ kW}$$

(d) What is the magnitude of the current flowing in each phase of the generator and in the transmission line?

1

$$I_{gen} = 0.4765 \times 120.28 = 57.3 \text{ A}$$

1

$$I_{TL} = 0.4765 \times 40.09 = 19.1 \text{ A}$$

3. A 300V shunt dc motor with $R_a = 0.15 \Omega$, $R_F = 40 \Omega$, $R_{adj} = 20 \Omega$. It draws a total current of 105A while running at a speed of 1200rpm. Neglect rotational losses.

7marks

(i) Calculate the **Torque** and **Efficiency** at this speed

$$I_F = \frac{300}{20+40} = 5 \text{ A}$$

$$I_a = 105 - 5 = 100 \text{ A}$$

$$E_a = 300 - 100 \times 0.15 = 285$$

$$T = \frac{285 \times 100}{1200 \times \frac{2\pi}{60}} = 226.8$$

$$\eta = \frac{285 \times 100}{300 \times 105} = 90.47\%$$

(ii) The resistance R_{adj} is removed while the load torque is reduced to 75% of its original value. Calculate the **new speed** and the **new efficiency**. Consider that the motor operates in the linear region of the characteristics.

$$I_{F2} = \frac{300}{40} = 7.5 \text{ A}$$

$$E_{a2} = 300 - I_{a2} \times 0.15$$

$$\frac{E_{a2}}{E_{a1}} = \frac{I_{F2}}{I_{F1}} \cdot \frac{n_2}{n_1}$$

$$\frac{E_{a2}}{285} = \frac{7.5}{5} \cdot \frac{n_2}{1200}$$

$$\frac{T_1}{T_2} = \frac{I_{F1}}{I_{F2}} \cdot \frac{I_{a1}}{I_{a2}} = \frac{1}{0.75} = \frac{5}{7.5} \times \frac{100}{I_{a2}}$$


$$I_{a2} = 50 \text{ A}$$

$$E_{a2} = 300 - 50 \times 0.15 = 292.5 \text{ V}$$

$$n_2 = \frac{1200 \times 5}{7.5 \times 285} \times 292.5 = 821 \text{ rpm}$$

$$\eta = \frac{292.5 \times 50}{300 \times 57.5} = 84.78\%$$

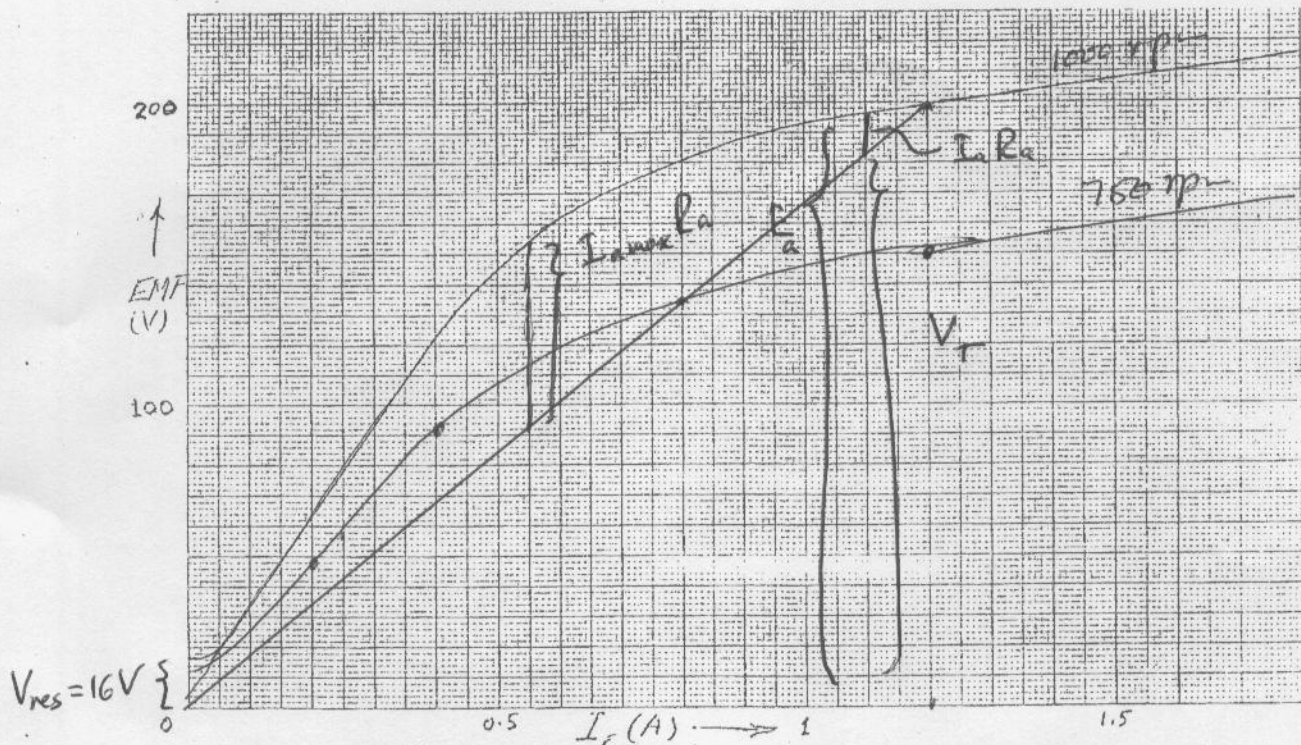4. A 9KW, 180V, 1000rpm shunt dc generator has an armature resistance $R_a = 0.3\Omega$ and a shunt field winding resistance of 60Ω . The characteristics of the machine is shown below. Neglect the armature reaction. 7marks



(i) Find the field control (external resistance) necessary to make the no load induced emf = 200V when the generator operates as a shunt generator.

$$\frac{200}{1.2} = 166.6 \Omega$$

$$\rightarrow 166.6 - 60 = 106.6 \Omega$$

$$\frac{9000}{180} = 50 \text{ A}$$

$$50 \times 0.3 = 15 \text{ V}$$

$$\rightarrow E_a = 197 \text{ V}$$

$$\rightarrow V_T = 182 \text{ V}$$

$$I_{R_{\max}} = 60 \text{ V} = I_{\max} \times 0.3$$

$$\rightarrow I_{\max} = 200 \text{ A}$$

$$\rightarrow \rightarrow R_{\text{critical}} = \frac{120}{0.4} = 300 \Omega$$

$$\rightarrow I_{sc} = \frac{16}{0.3} = 53.3 \text{ A} = \frac{V_{res}}{R_a}$$

\rightarrow Critical Resistance is the shunt resistance above which no emf is induced in the armature