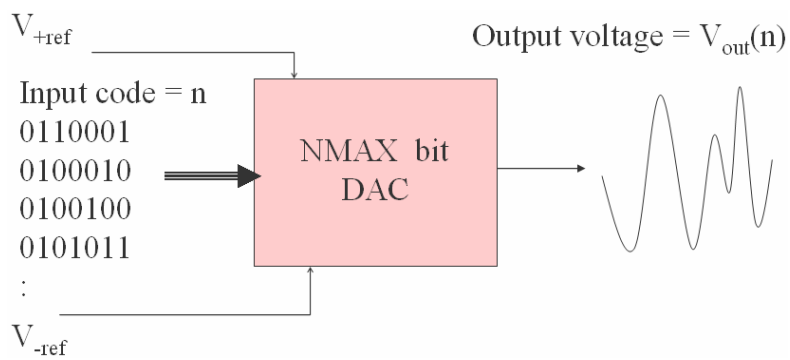


The Digital-to-Analogue Conversions (DAC) and Analogue-to-Digital Conversion (ADC)

Slide 1

Digital to Analogue Conversion




Slide 2

Digital to Analogue Conversion

- V_{+ref} , V_{-ref} are the high, low reference voltages respectively, $NMAX$ =bit length of the DAC, n is the input code.

$$V_{out}(n) = V_{-ref} + n \left[\frac{V_{+ref} - V_{-ref}}{2^{NMAX}} \right]$$


$$= V_{-ref} + n\Delta V$$

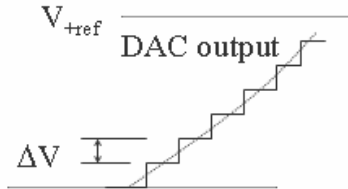


- At $n=0$, $V_{out}(0) = V_{-ref}$
- At max. $n = 2^{NMAX} - 1$, V_{out} cannot reach V_{+ref} , (e.g., for $NMAX=4$, $n=0,1,2,..15$)
- Some DACs have internal reference voltage settings, some can be set externally.

Slide 3

The DAC0830

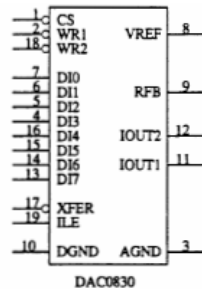


The Pin-Out

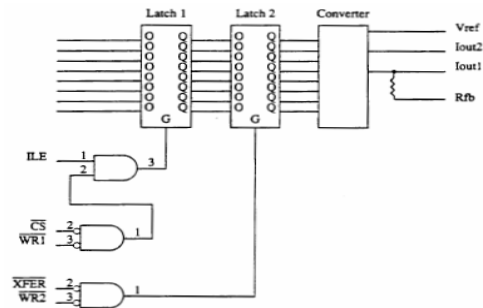

The internal circuit


Slide 4

The DAC0830 Interface to the Microprocessor

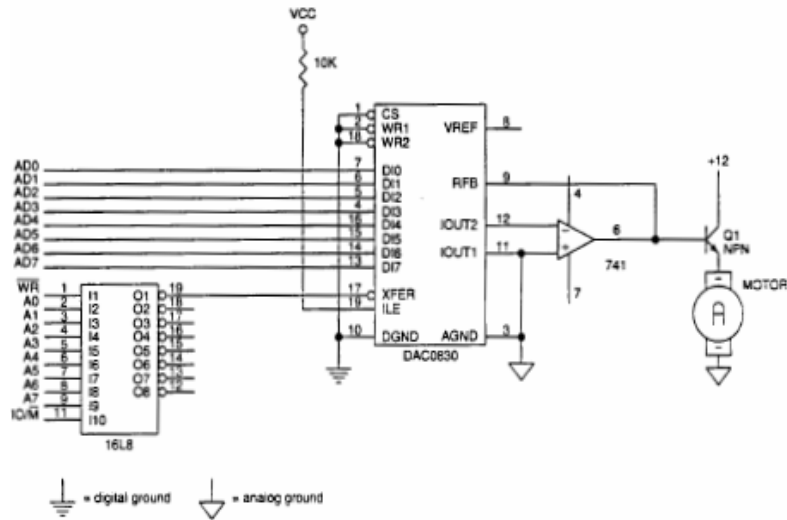

Slide 5

Analogue to Digital Conversion

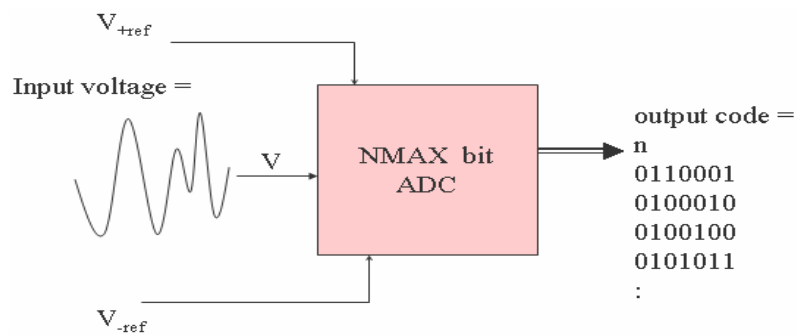


Slide 6

Analogue to Digital Conversion

● n = converted code, V = input voltage,



$$n = \left[\frac{V - V_{-ref}}{\Delta V} + \frac{1}{2} \right]_{\text{integer}}, \text{ where } \Delta V = \frac{V_{+ref} - V_{-ref}}{2^N - 1},$$

e.g., $V_{-ref} = 0$, $\Delta V = 10 \text{ mV}$, as shown below :

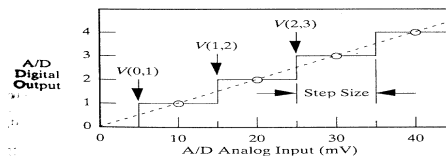

Slide 7

The ADC0804

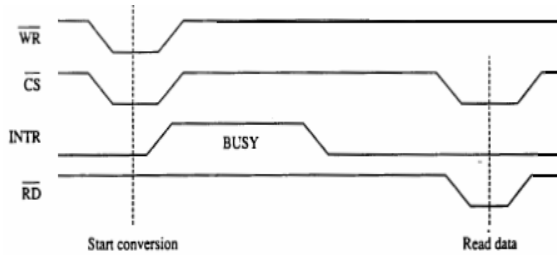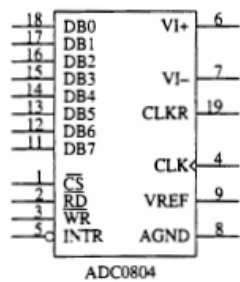


Timing Diagram

Slide 8


The Analogue Input to the ADC0804



(a) To sense a 0- to +5.0-V input.

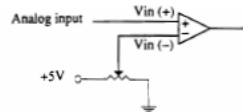

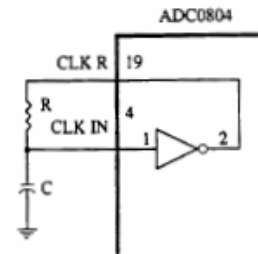(b) To sense an input offset from ground.




Connecting the RC circuit to the CLK IN and CLK R pins on the ADC0804.

$$F_{clk} = \frac{1}{1.1 RC}$$


Slide 9

The Analogue Interface to the Microprocessor

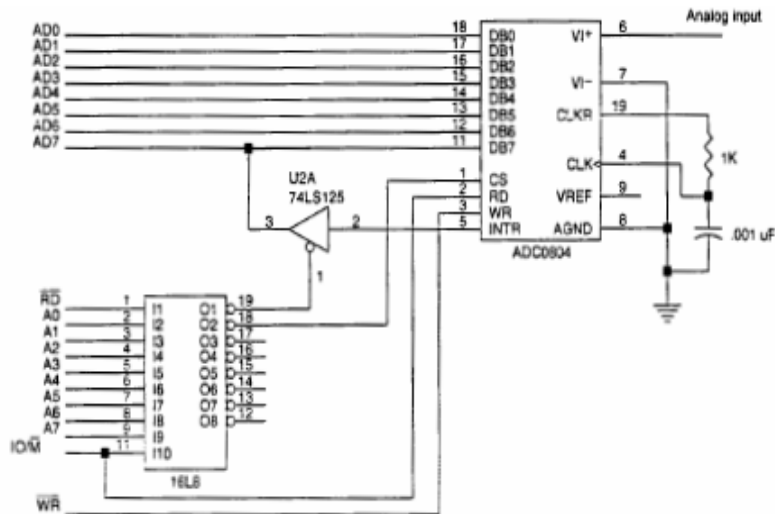

Slide 10

Application Example

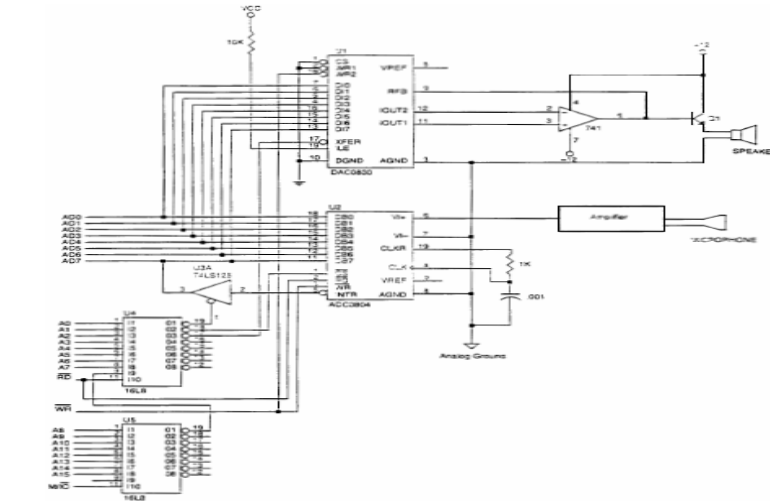

Slide 11